

図6. 1 RC回路の過渡応答

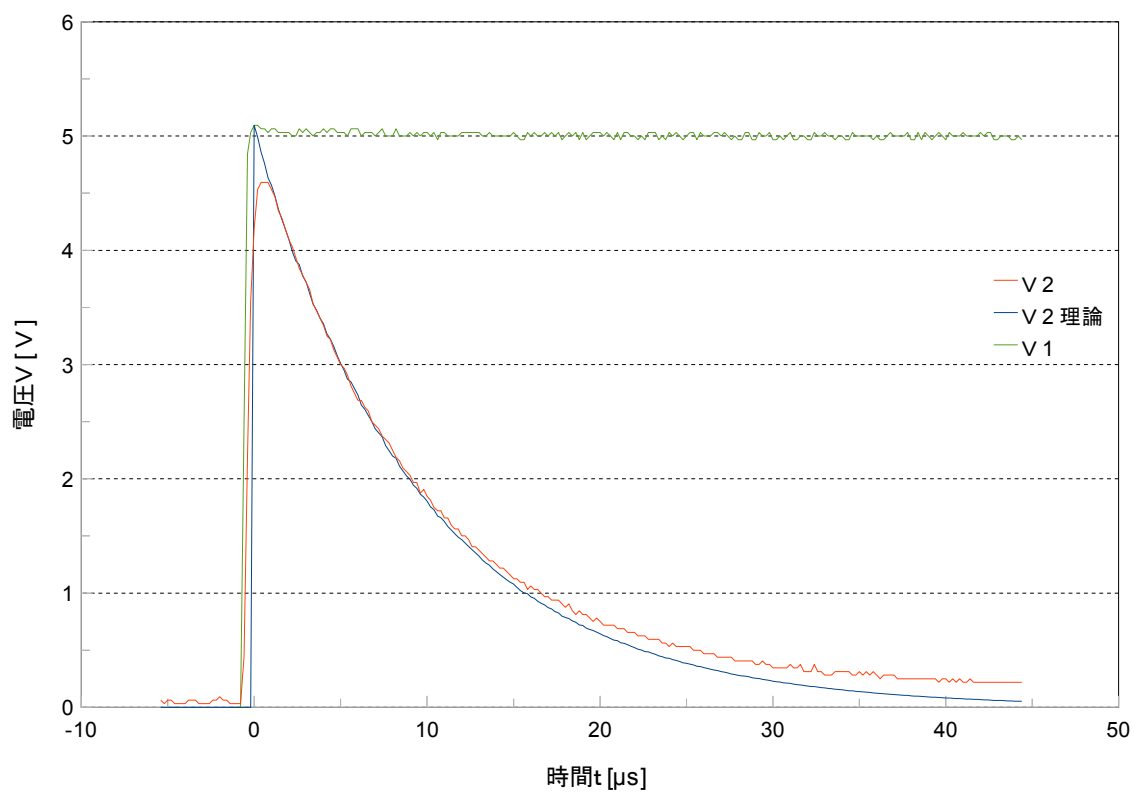


図6. 2 RL回路の過渡応答

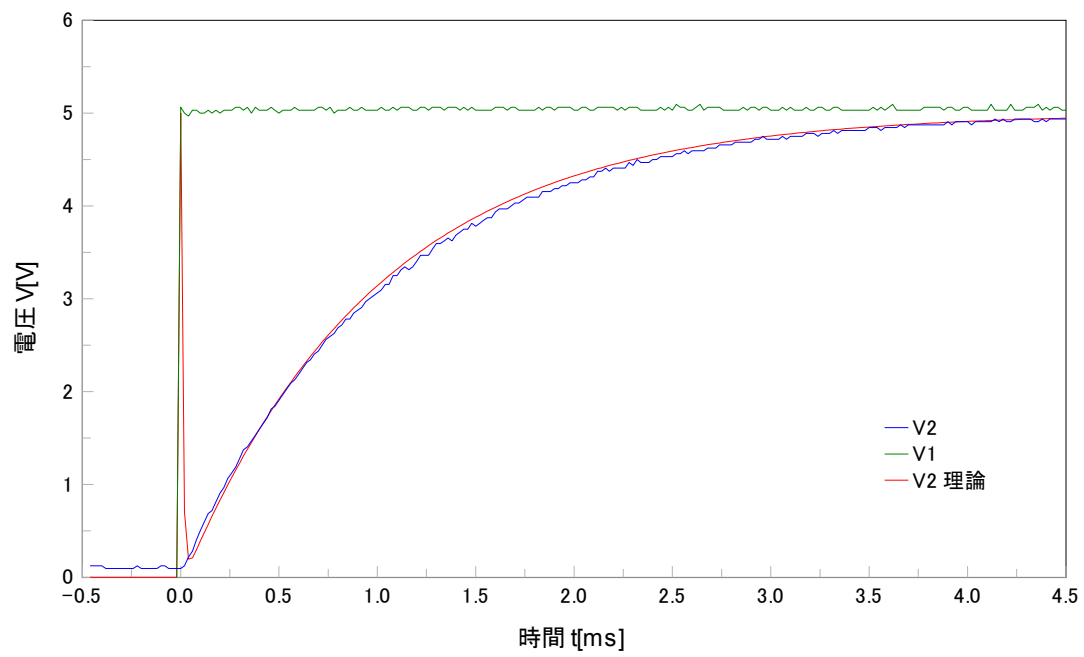


図6. 3 RLC回路の過渡応答(過制動)

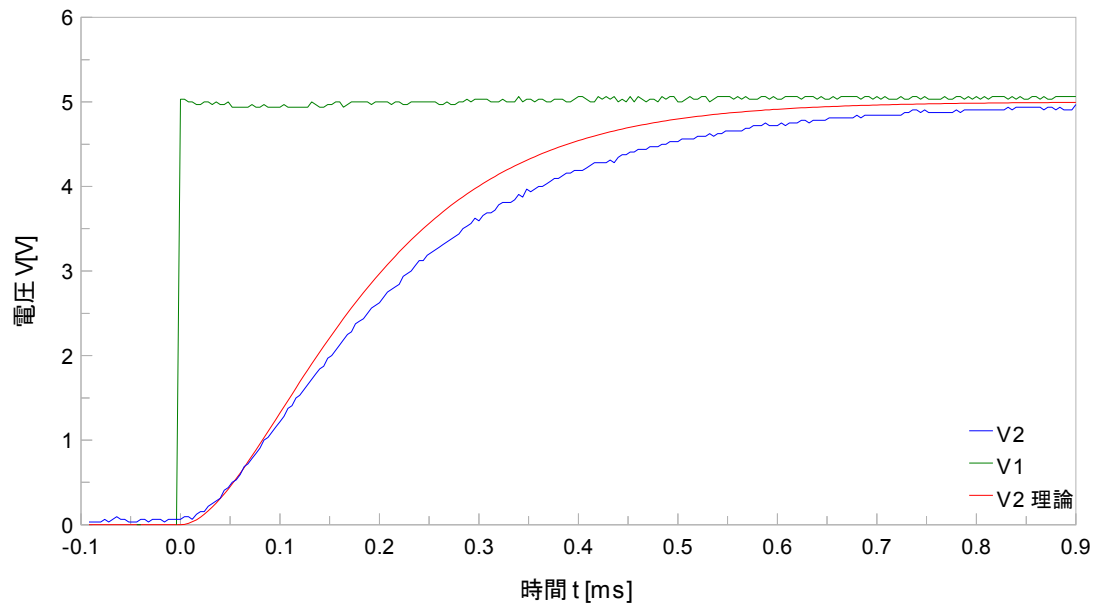


図6. 4 RLC回路の過渡応答(臨界制動)

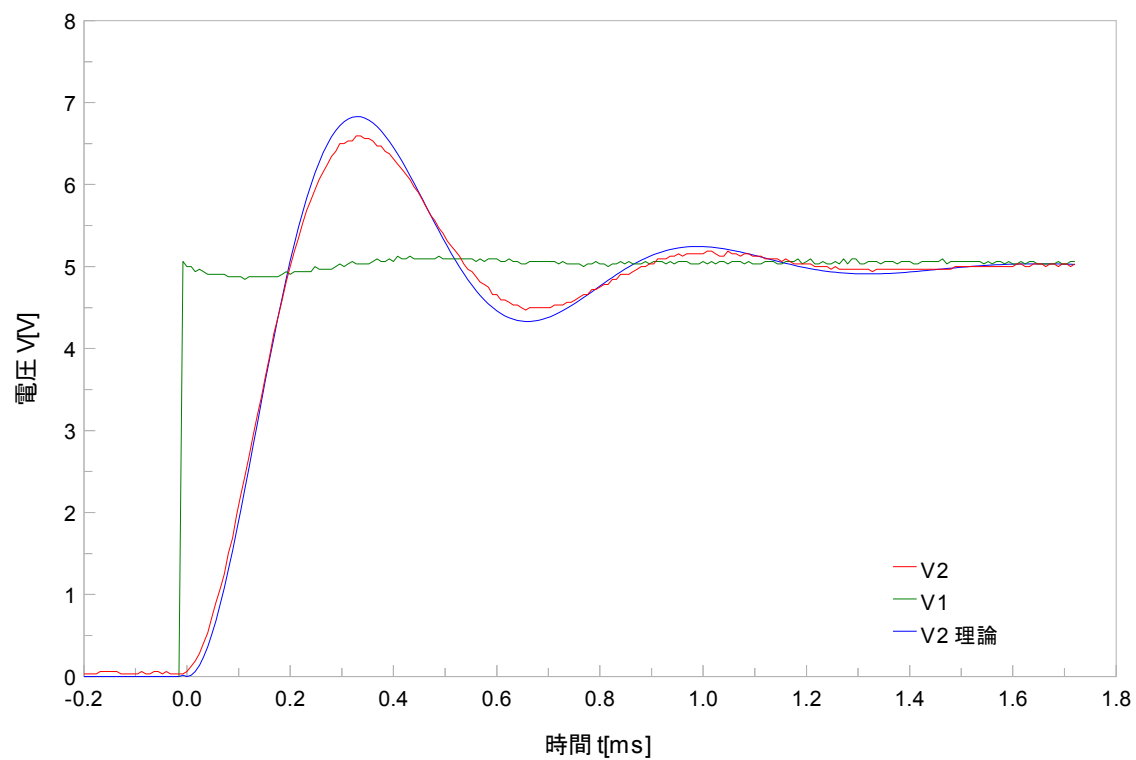


図6. 5 RLC回路の過渡応答(不足制動)